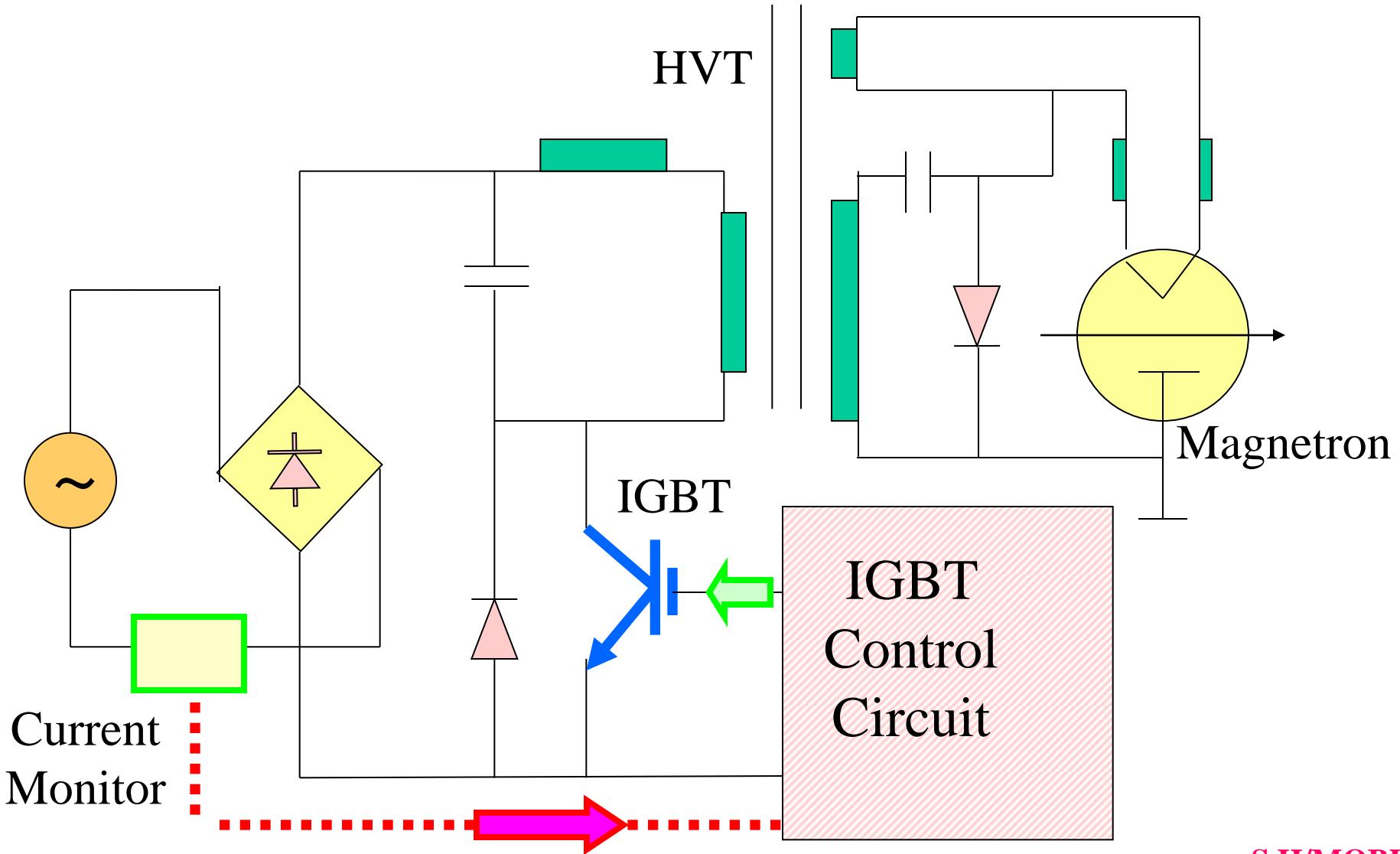


*M300 Inverter
Power Supply
Circuit &
Troubleshooting*

Basic Inverter Circuit




Why IGBT Employed?

Bipolar
Transistor



Big drive power required
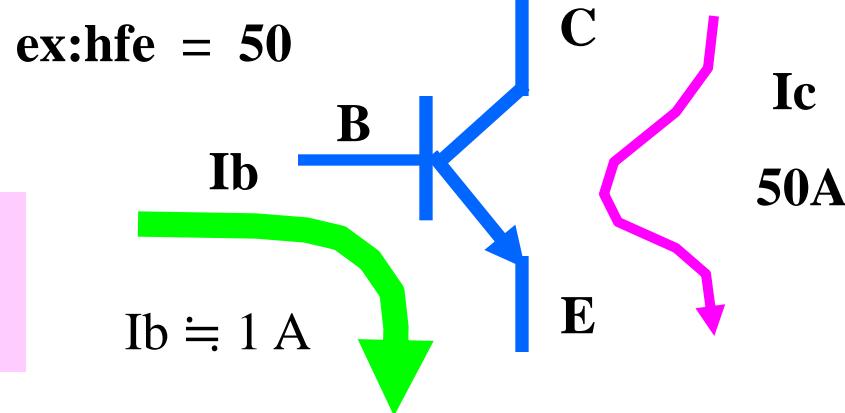
$$20 \text{ V} \times 1 \text{ A} = 20 \text{ W}$$




Isolated Gate Bipolar
Transistor IGBT

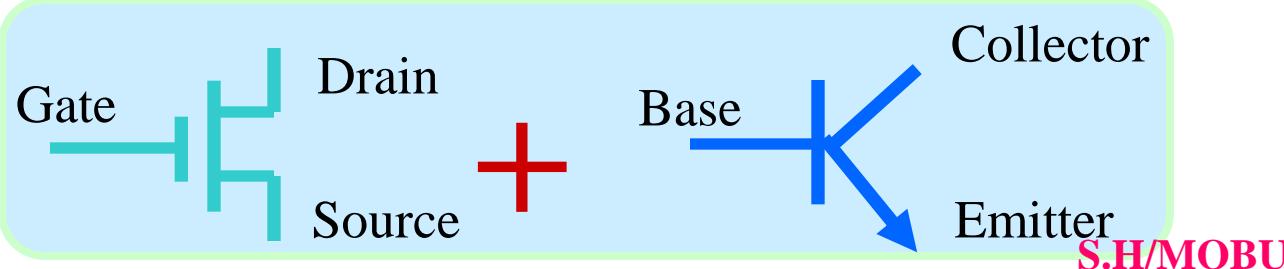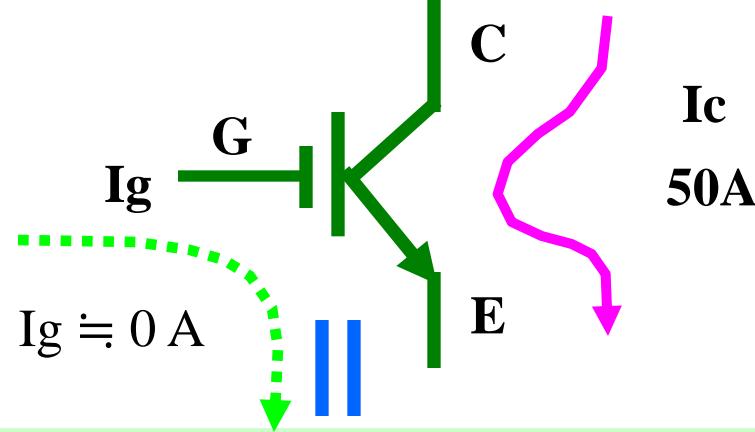
No need of drive power
just need voltage drive only
 $20 \text{ V} \times 0 \text{ A} = 0 \text{ W}$



Block Diagram of Inverter Circuit

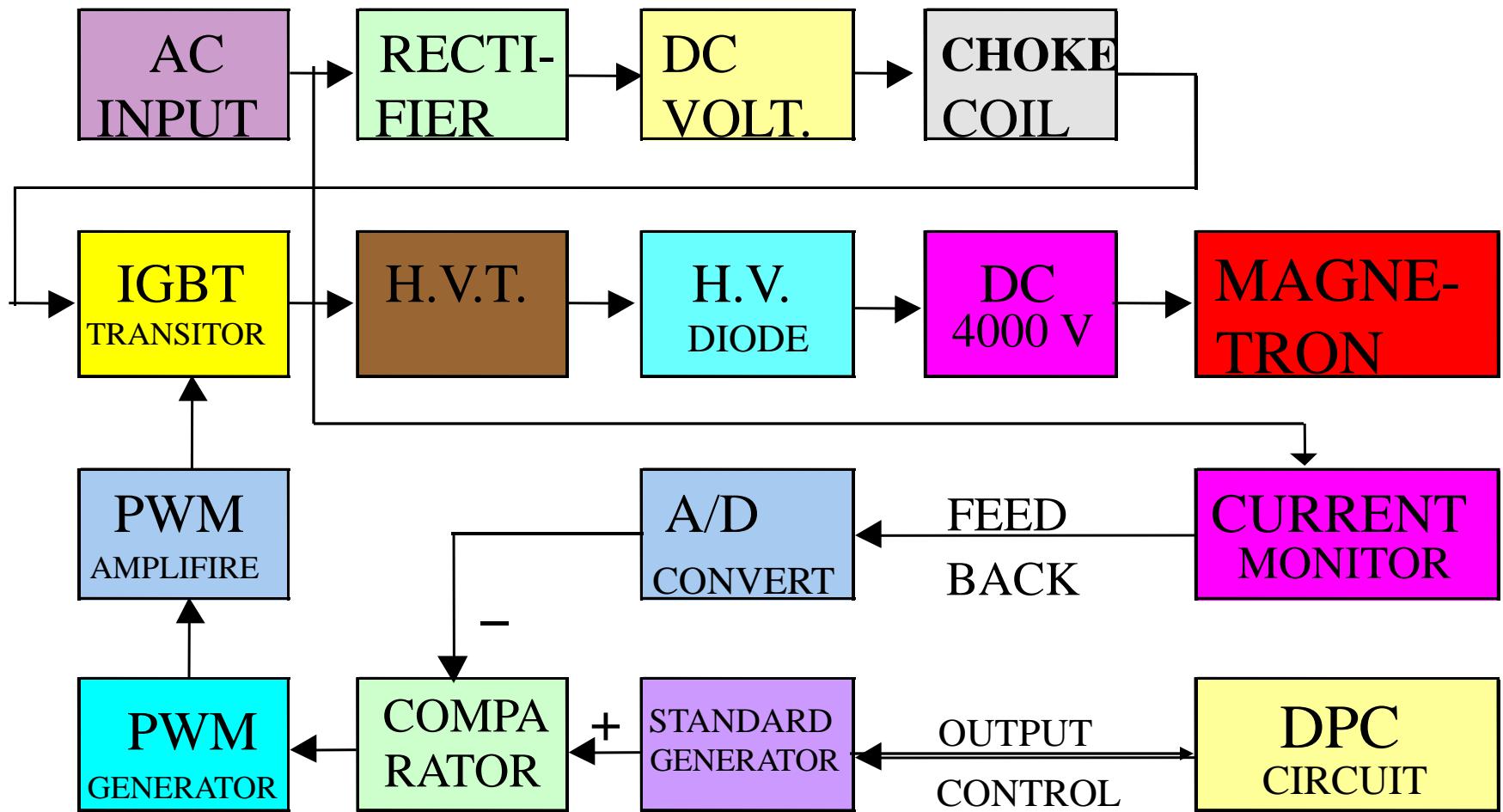


Inverter PCB Schematic Diagram

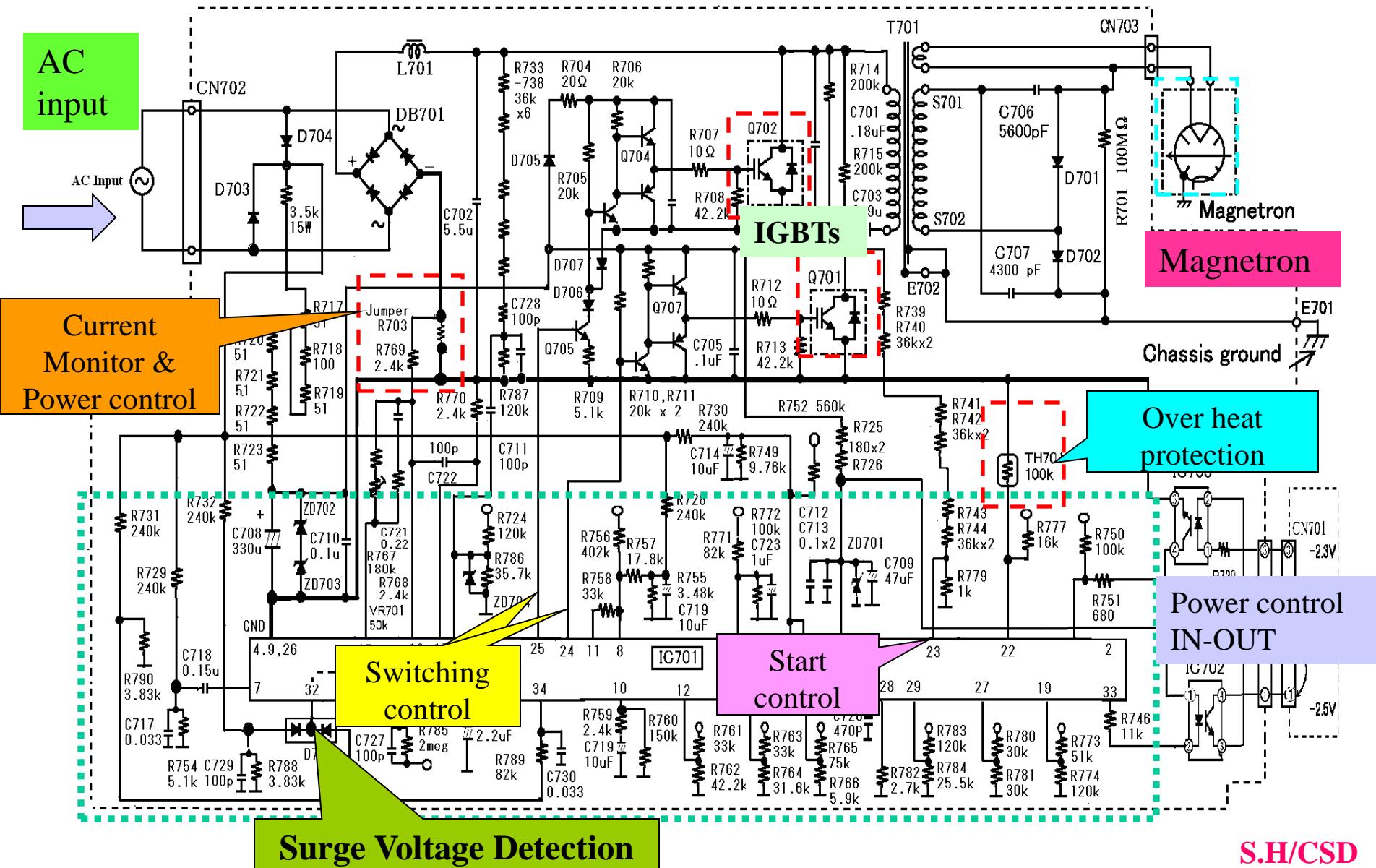

S.H/CSD


Schematic Diagram/Inverter IGBT area

Q702 High side IGBT

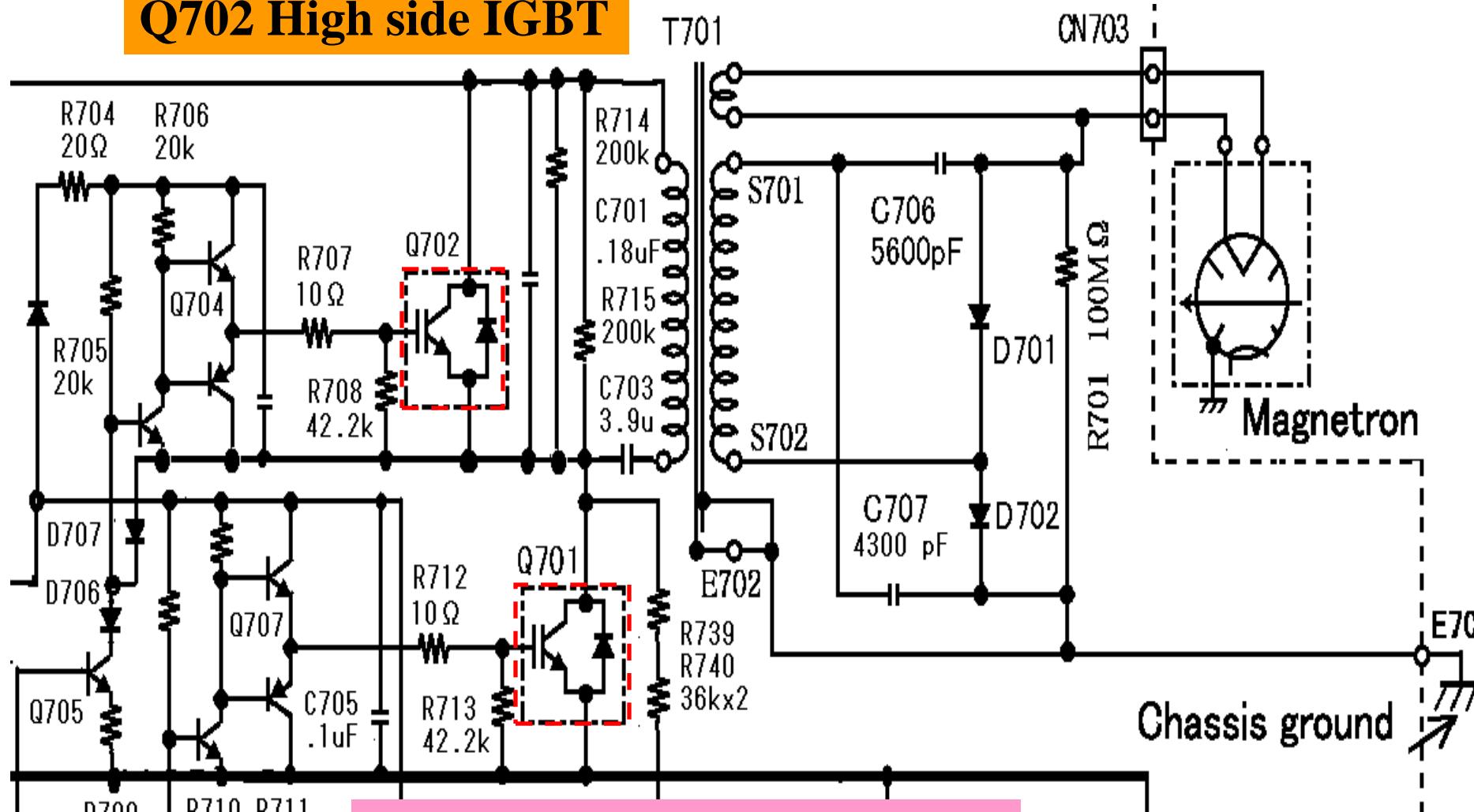

Q701 Main Switching IGBT

IGBT Switching Circuit

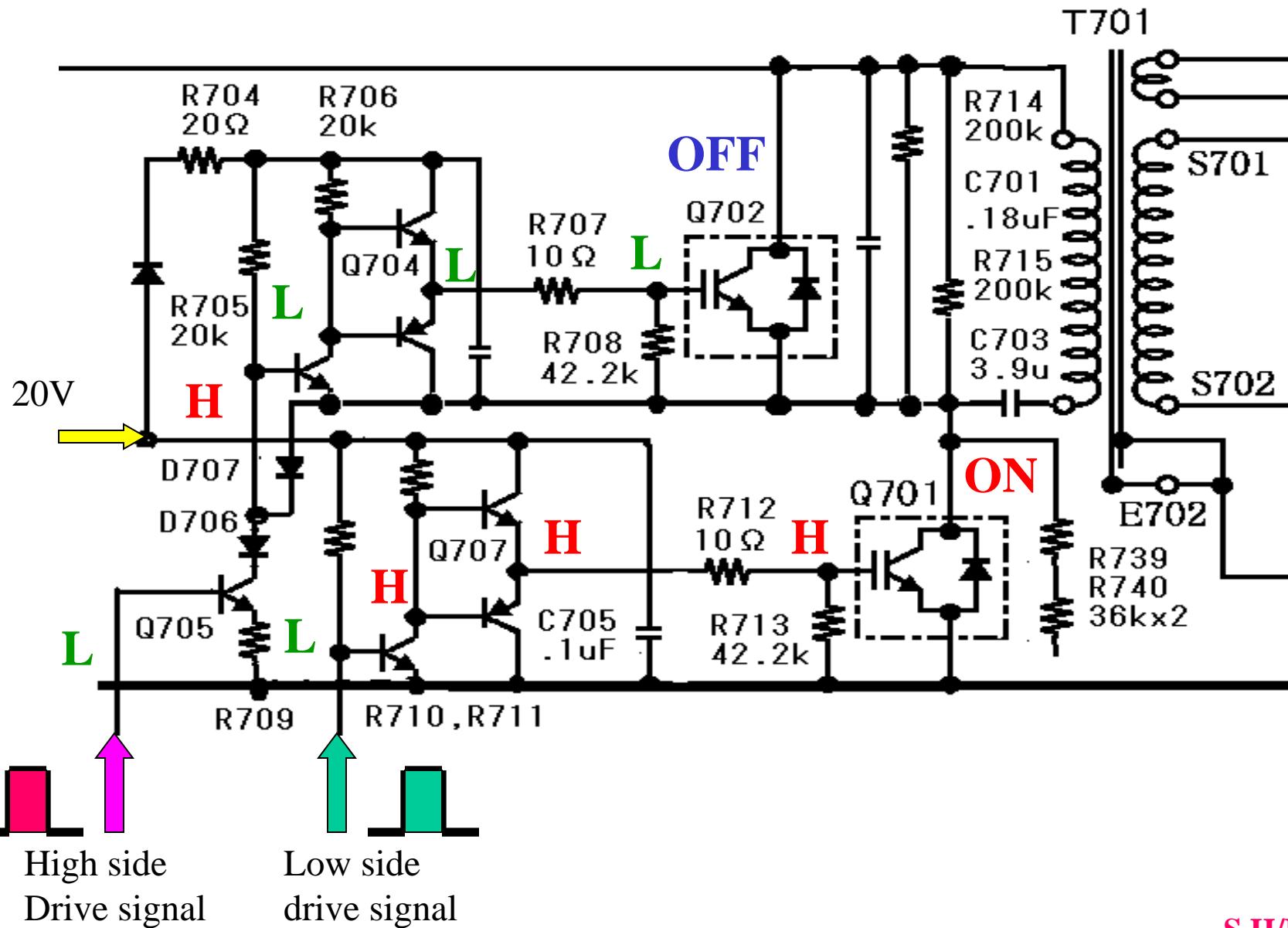


Power Control

Circuit and


It's Operation

New Current Monitor Circuit

AC
230/240V
input

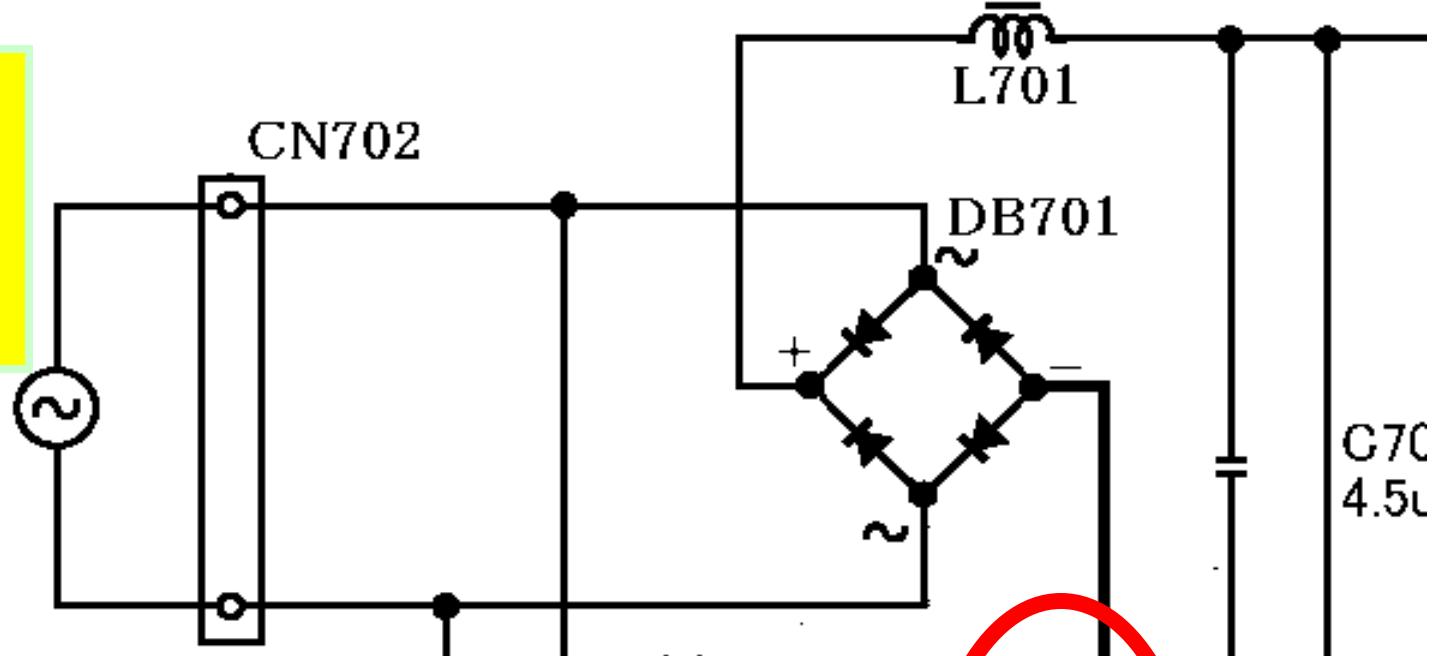


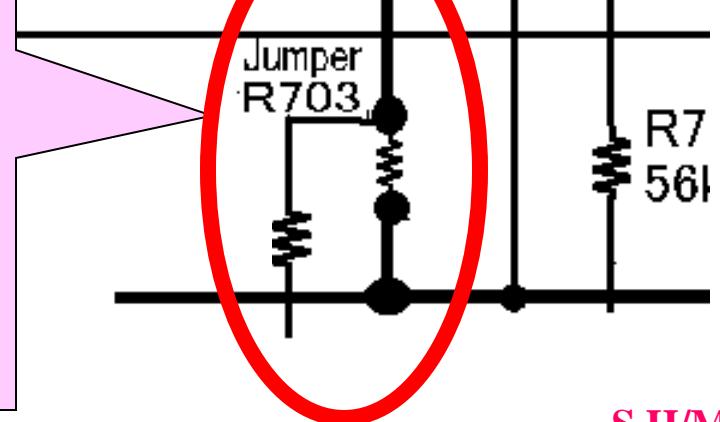**R703 Jumper wire.
Monitor AC Input Amps
by voltage readings across
R703.(under heat sink)**




Current Monitor Circuit

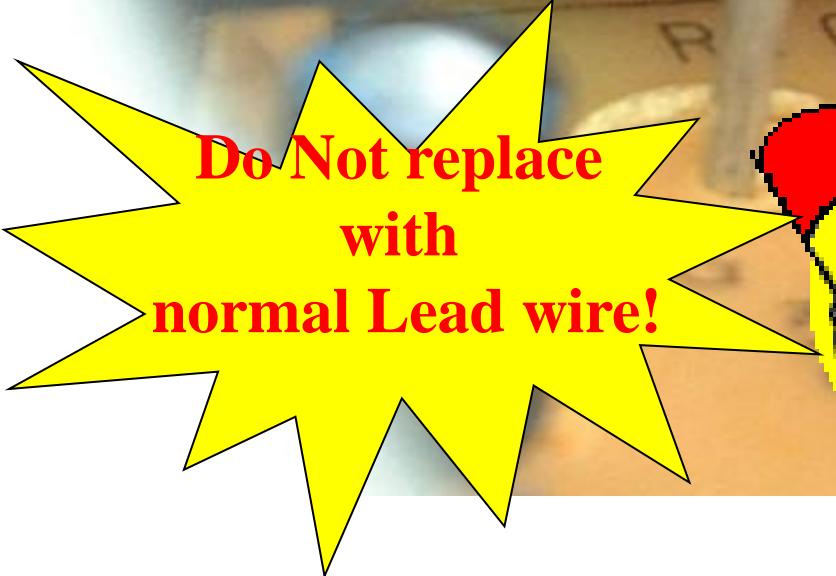**R703 is Specially designed Resistance
wire not just a normal copper lead wire**



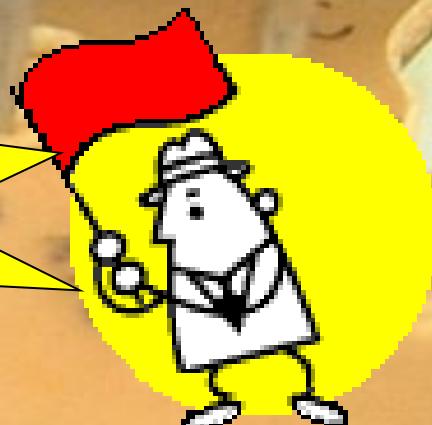
**Do Not replace
with
normal Lead wire!**



0.4 Ω/m resistance wire
which become approx.
10 m Ω as R703. M300 type


M300

Current Monitor Circuit

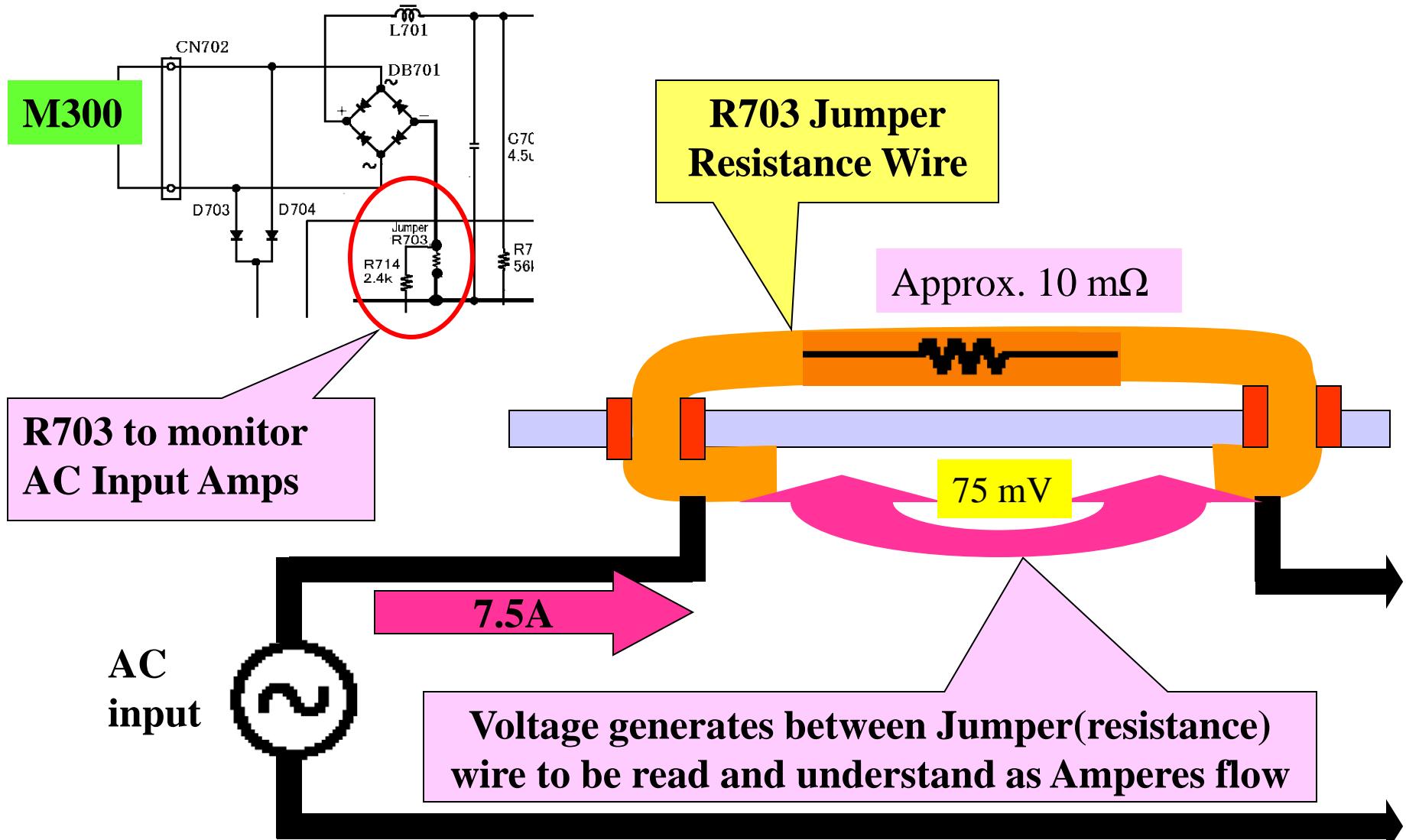

Output Adjustment Volume

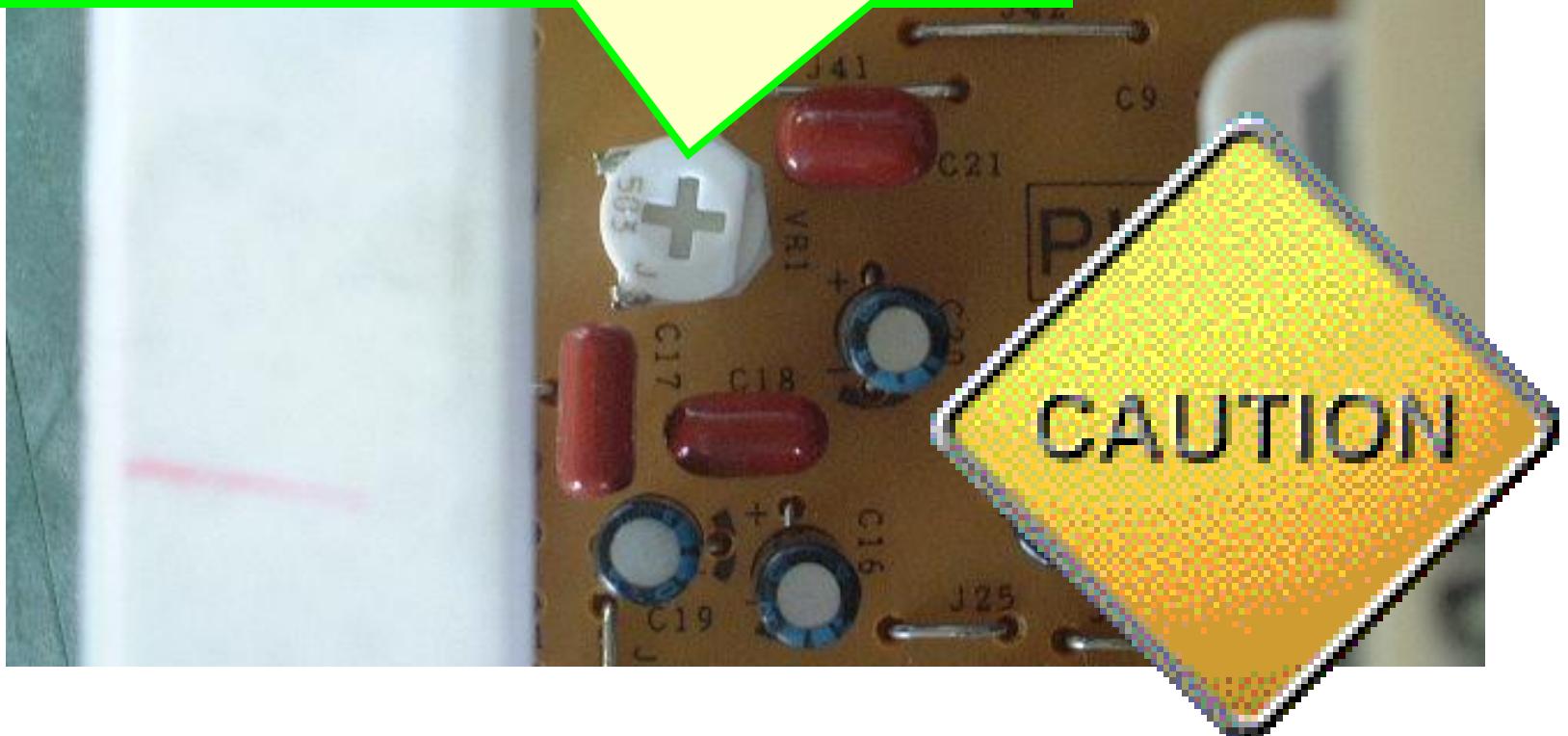Do not Adjust unless you have
Precise ammeter and knows
proper adjustment method.




CAUTION

HV Isolation Photo-Coupler IC

Inverter
HV side

Input

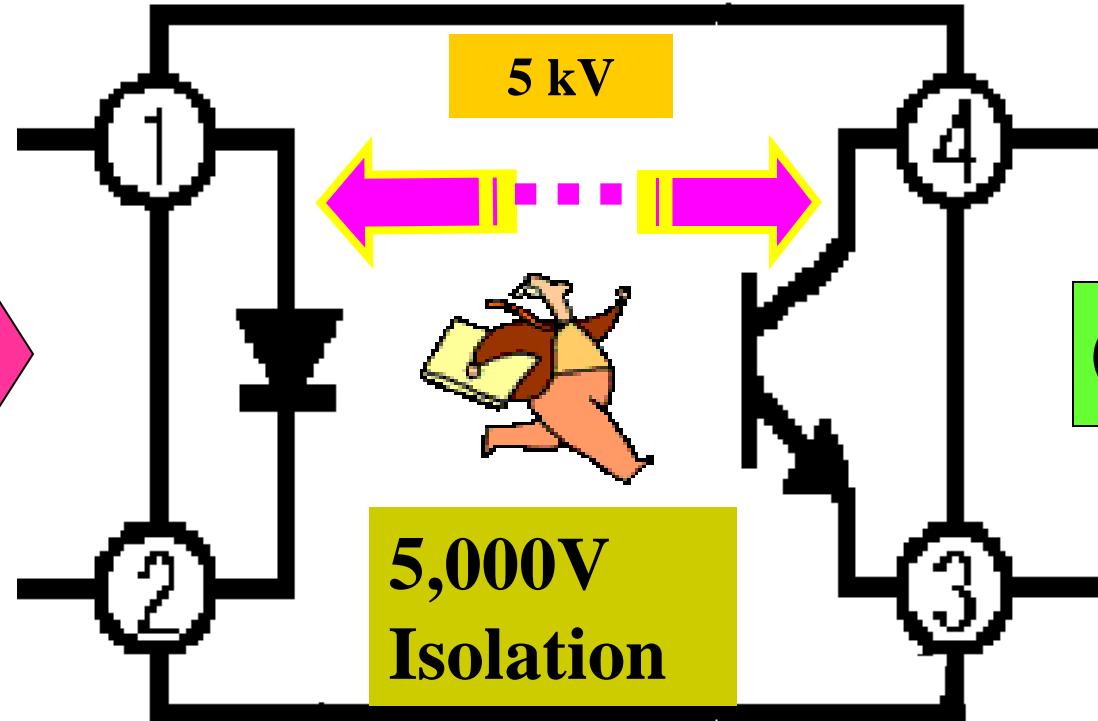


DPC
LV side

Output

To isolate 5 kV between High voltage Inverter
section and Low voltage DPC section

DPC and Inverter Control Circuit

Inverter side

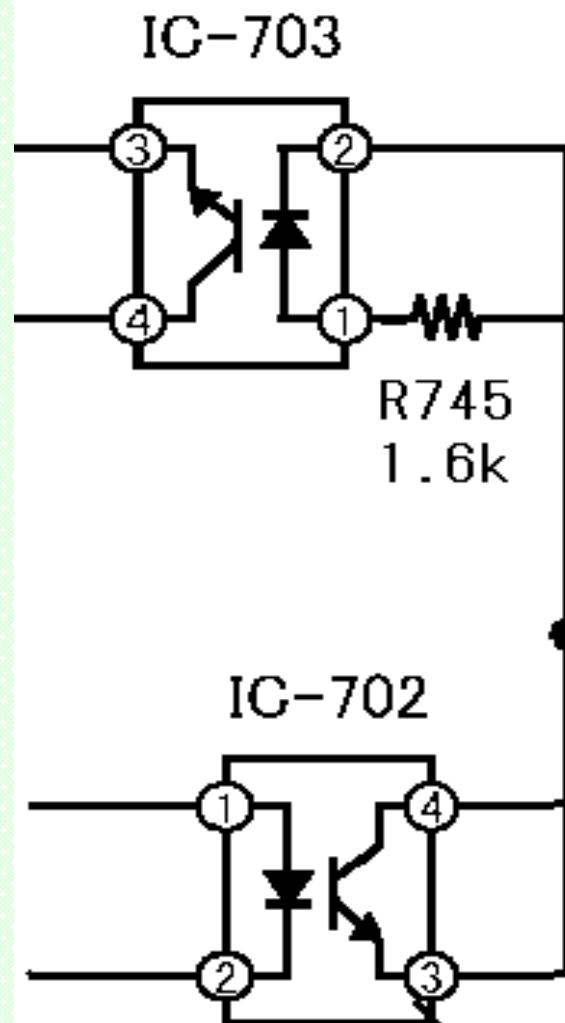

CN701

PWM signal

$f = 70 - 250$ Hz



$F = f/2$

Feedback signal

DPC side

5V P-P
+2.3V
rms

DPC


0V

+2.5V
rms

5V P-P

HV Isolation Photo-Coupler IC

5 KV each
Isolation

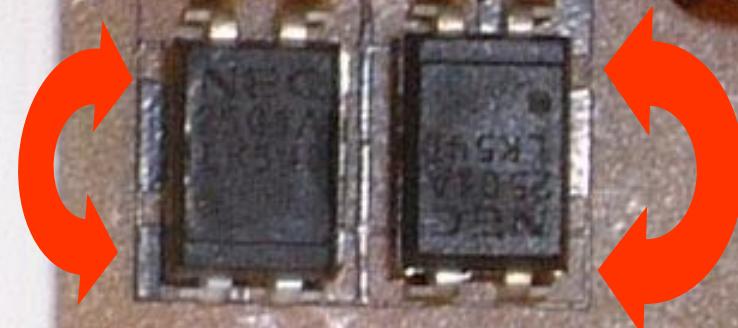


To DPC

Isolate between High voltage Inverter circuit section
and Low voltage DPC circuit section

DPC is Isolated from High Voltage


Signal flow between DPC and Inverter

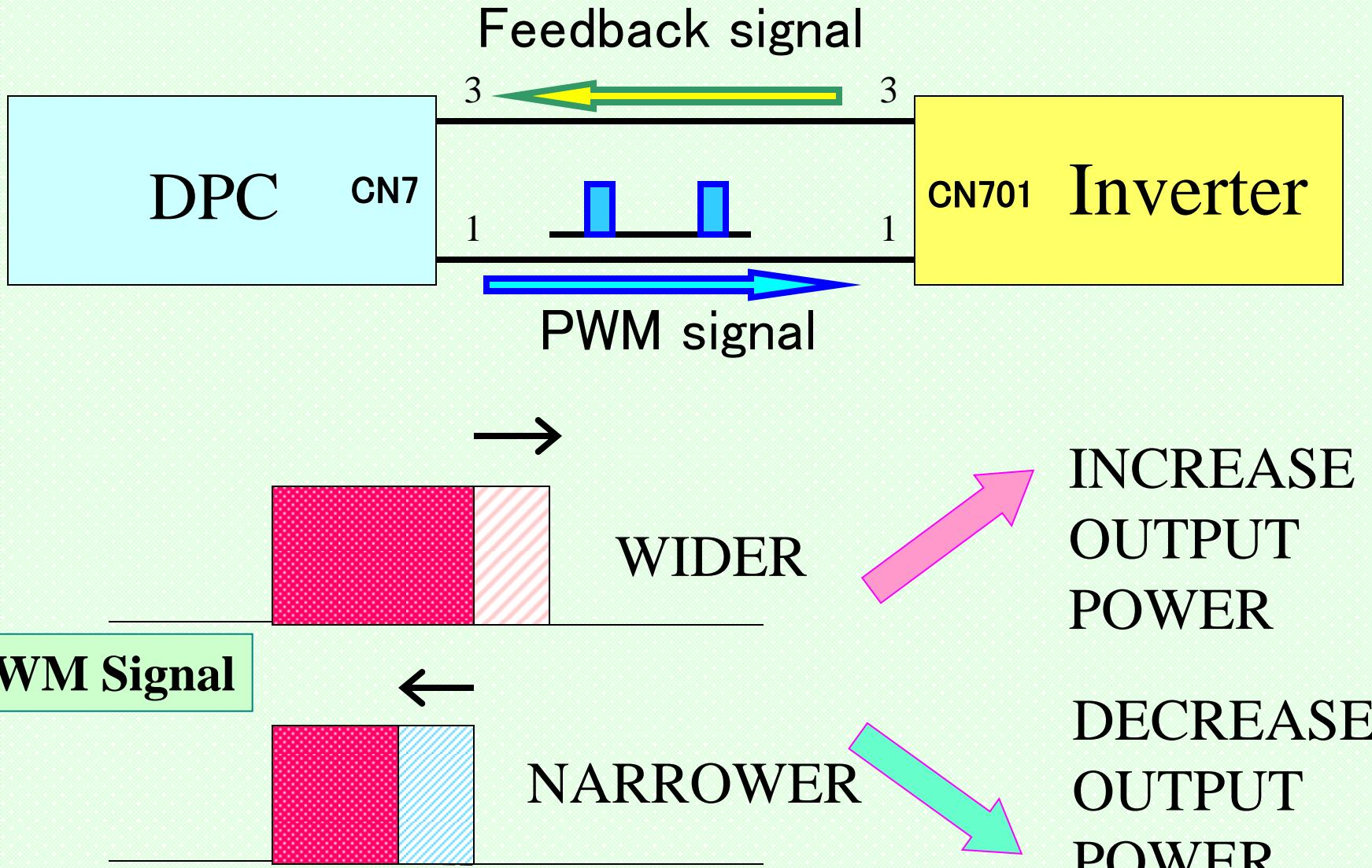

Inverter Circuit Troubleshooting


Troubleshooting Steps

1. Unplug Oven

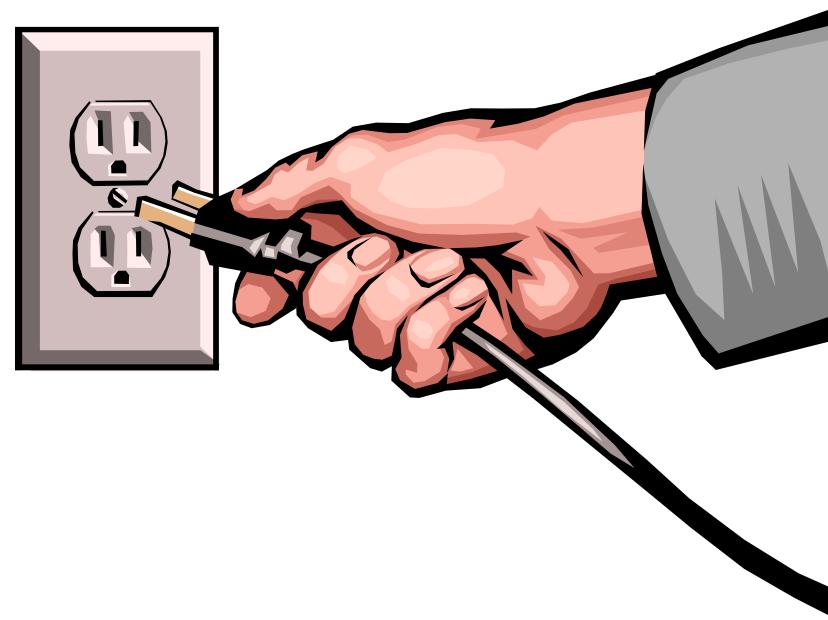


2. Discharge high voltages remaining in HVC in PCB

How to Discharge High Voltage Capacitors

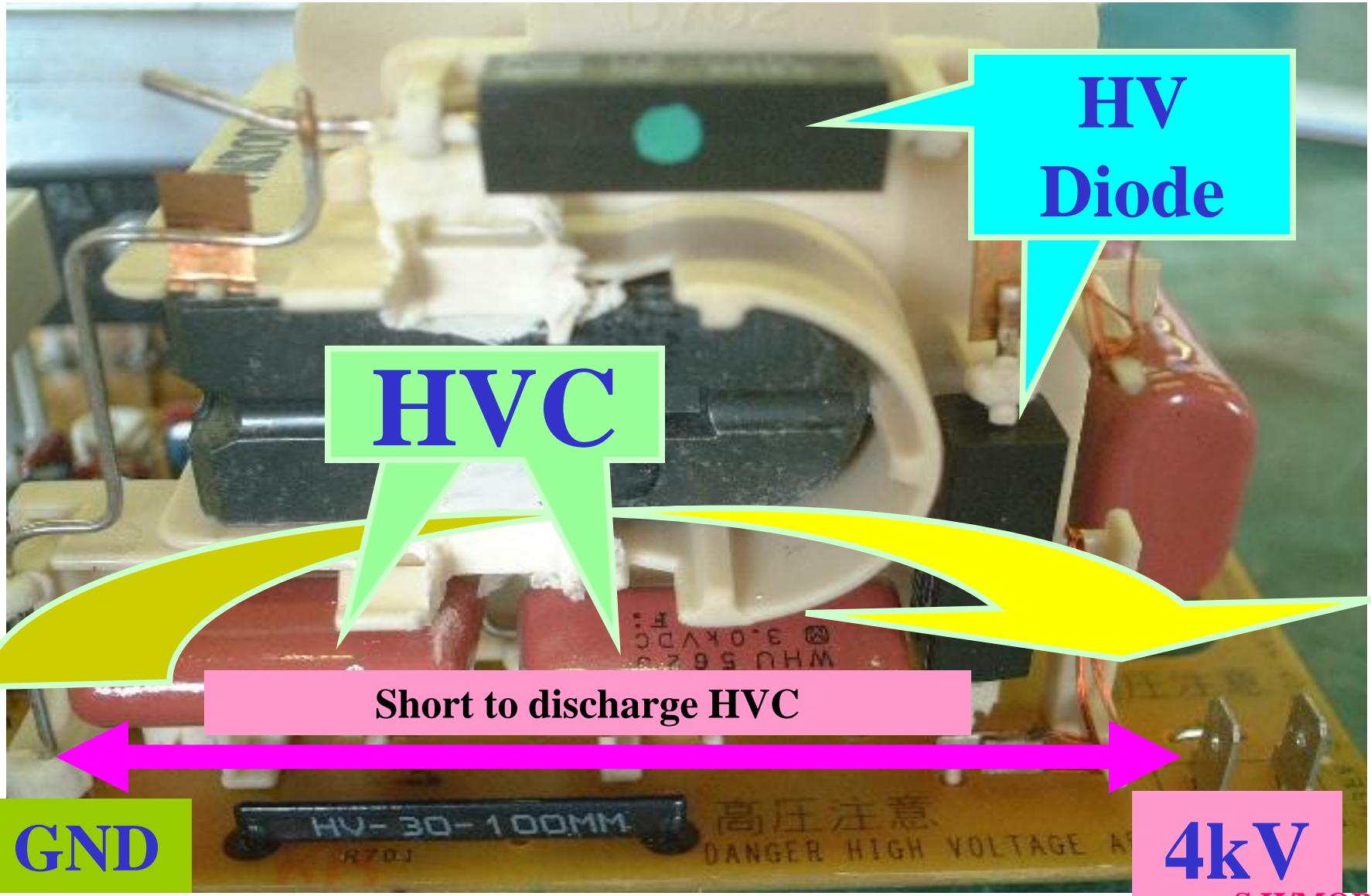

Troubleshoot work flow

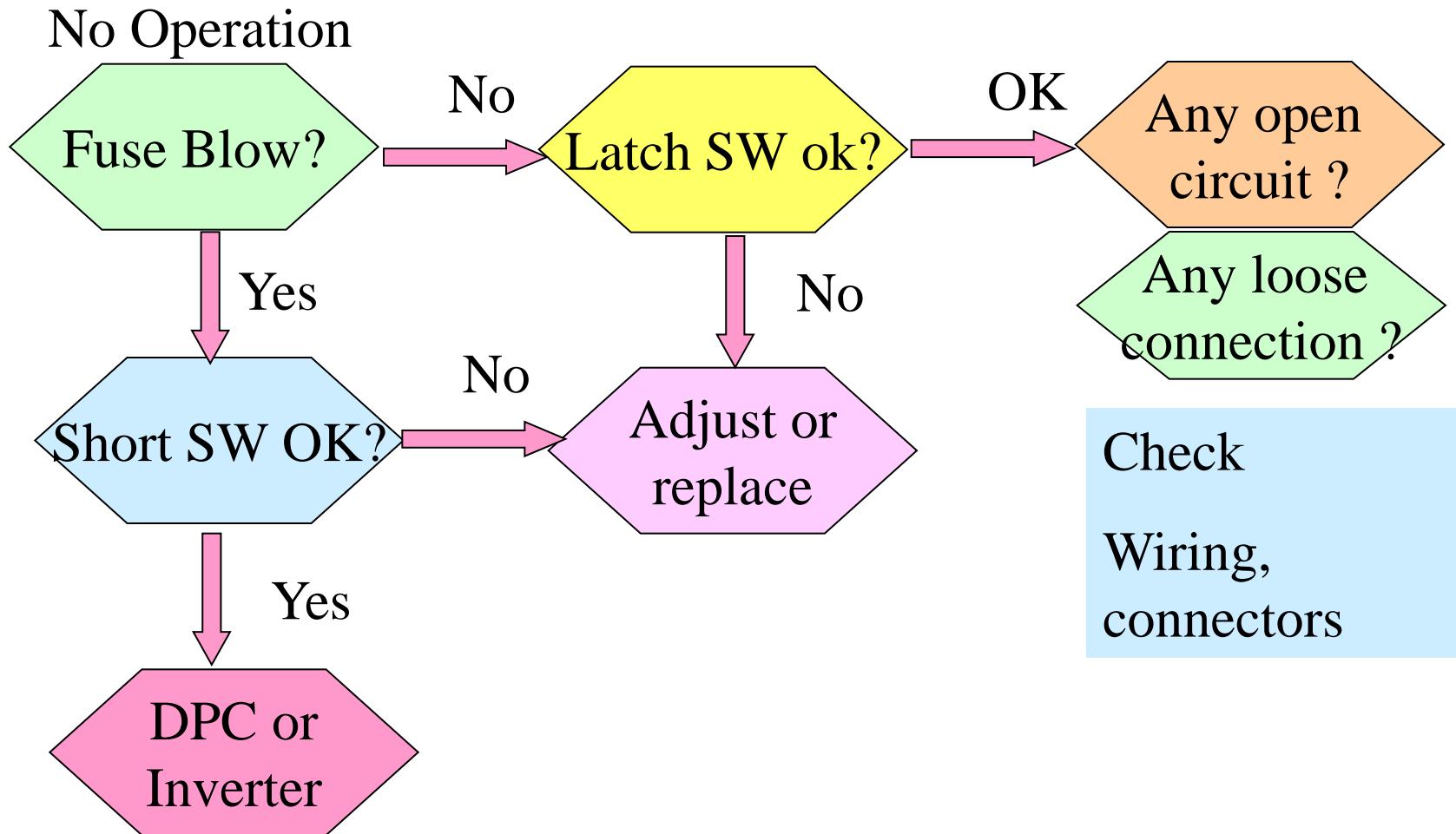

Q701,Q702,DB701 etc. Follow to next.....

3. Unplug all connectors and remove PCB from Oven


WARNING: Make sure to isolate PCB from Oven

Unplug connectors


AC input

Control

signals line

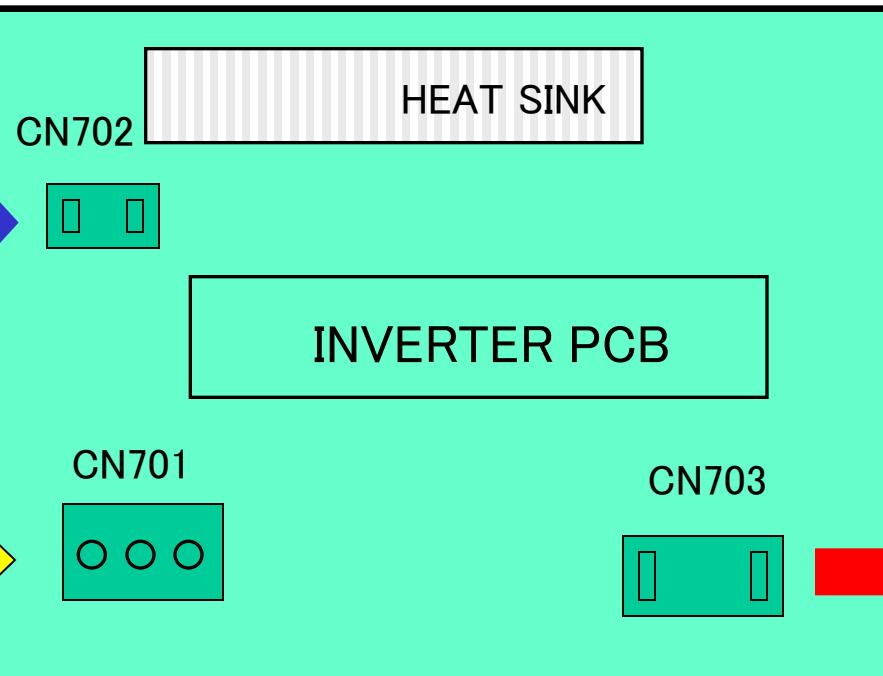

**DANGER
HIGH VOLTAGE**

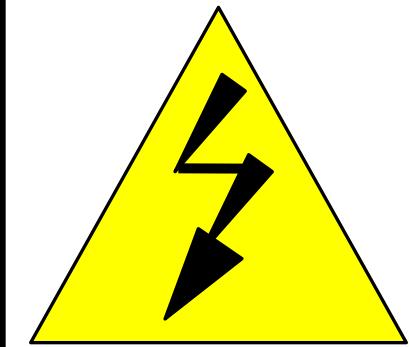

**DO NOT MEASURE
HIGH VOLTAGE**

**HIGH VOLTAGE
OUTPUT TO MAG**

4. Check Continuity across CN2 Connector pins


Check Across CN702 pins

80 – 200k Ω
is normal

Change Polarity

If it is smaller Ω

Follow Next step


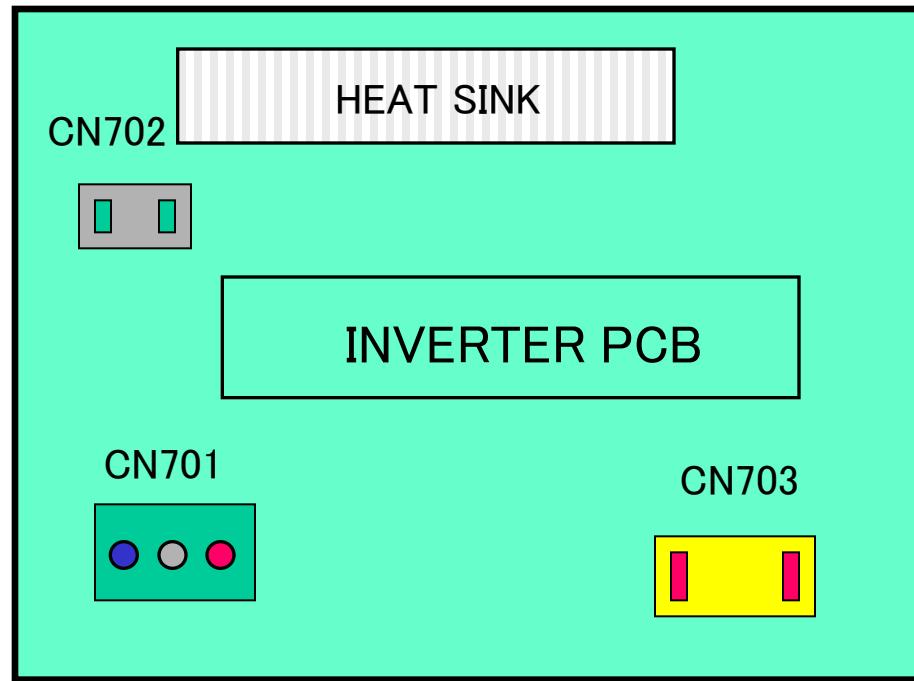


Check

Diode bridge, IGBT's &
High voltage diodes by
Ohm meter


NOTE: Make sure to check if the related circuit and components are any damaged such as burnt resistors.

5. How to Check Q701 & Q702

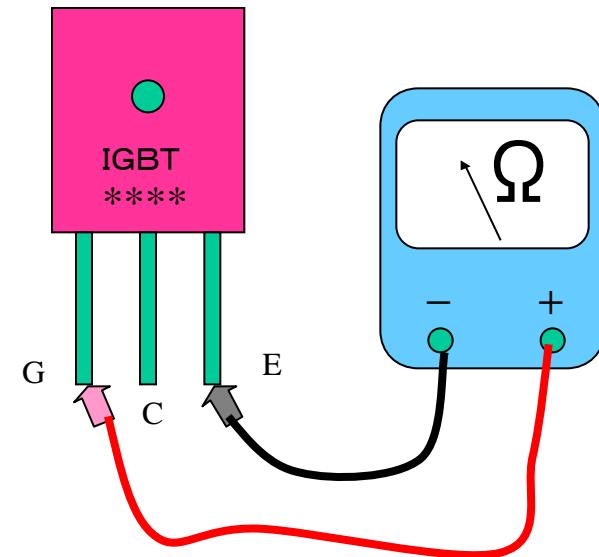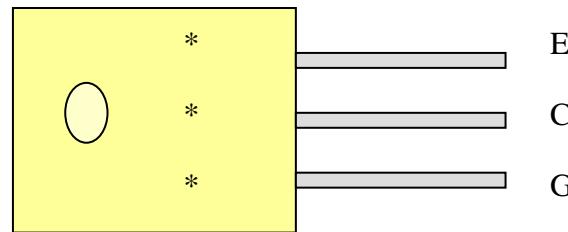


	Forward	Reverse
E-C	Some Ω	$\infty \Omega$
E-G	$\infty \Omega$	$\infty \Omega$
C-G	$\infty \Omega$	$\infty \Omega$

7. Check Bridged diode DB701

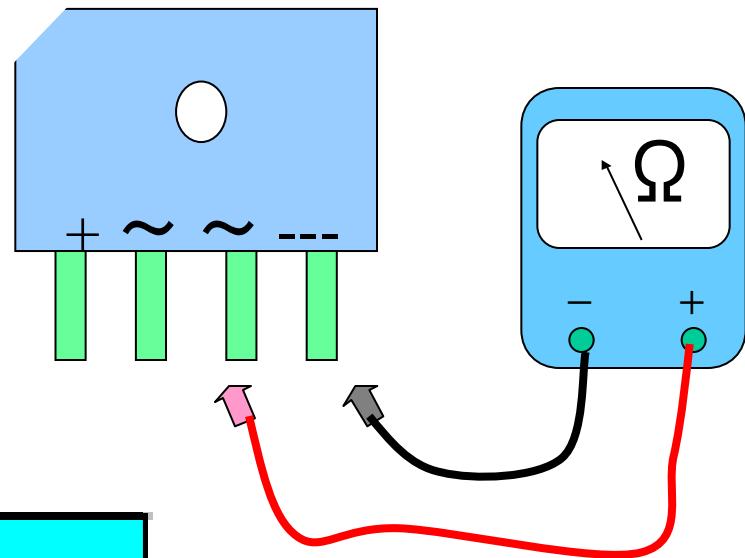

	Forward	Reverse
+ - -	Some Ω	$\infty \Omega$
$\sim - \sim$	$\infty \Omega$	$\infty \Omega$
+ - \sim , - - \sim	Some Ω	$\infty \Omega$


8. Check High Voltage Diodes

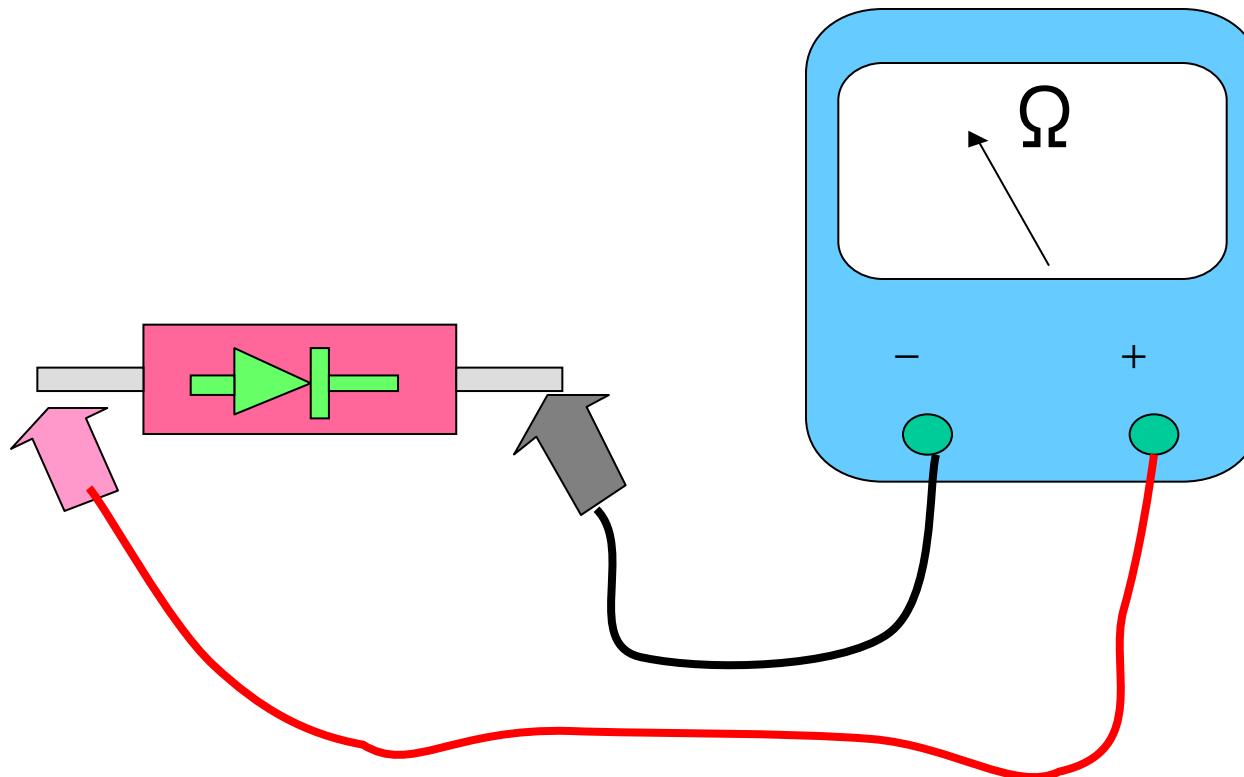

Forward	Reverse
Some Ω	$\infty \Omega$

Fault diode can be checked by even R X 1

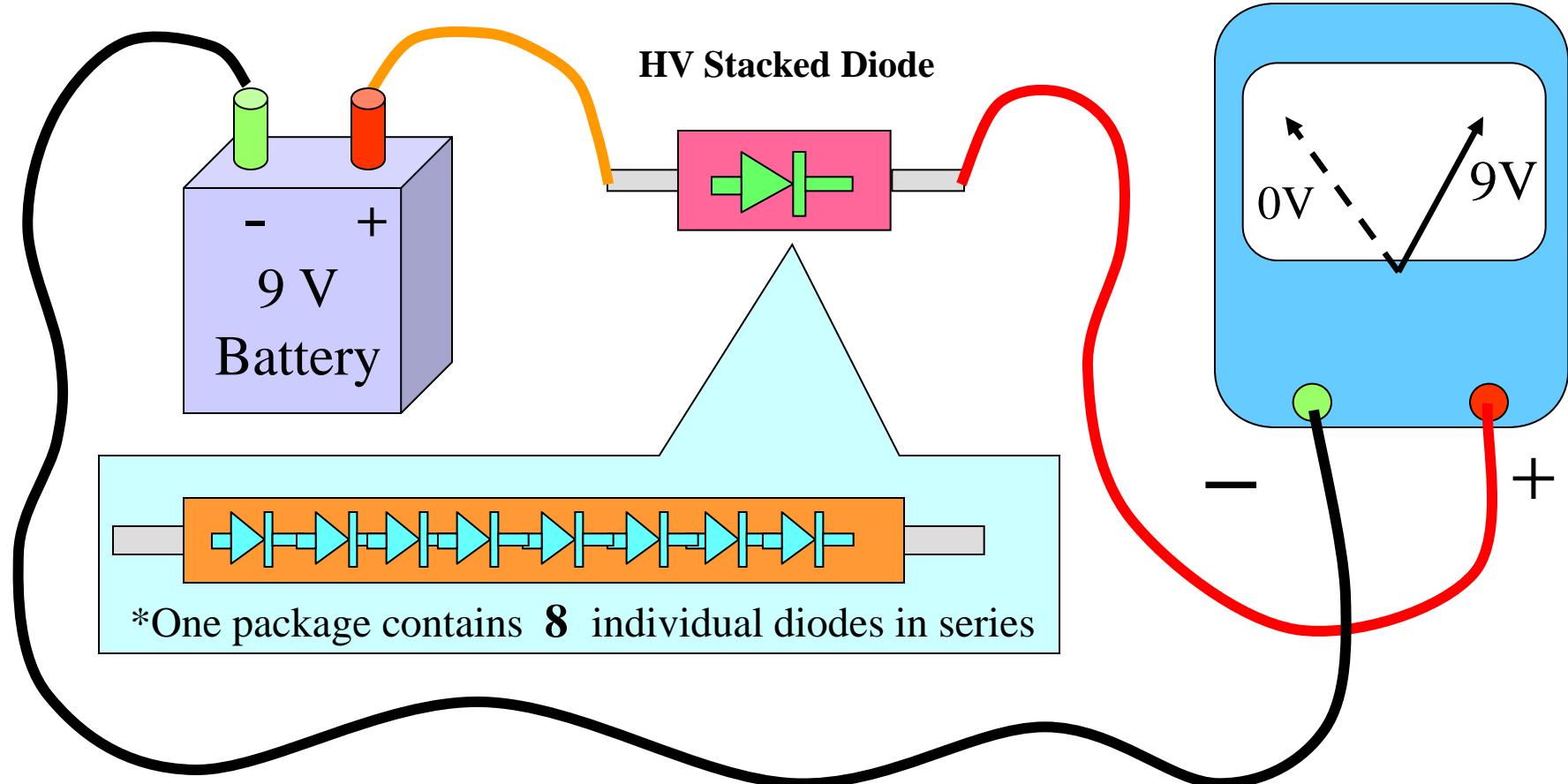9. Check High Voltage Diodes W/ 9V Battery




Forward	Reverse
9 Volts	0 Volt

Inverter PCB Defect Analysis

DB701,Q701,Q702	69	39.4%
R730	16	9.1%
R704	14	8.0%
R731	7	4.0%
R752	5	2.9%
R729	4	2.3%
C701	2	1.1%
R769	2	1.1%
Others	6	3.4%
OK	36	20.6%
Cracked	14	8.0%
Total	175	100%


Inverter PCB Fault Cause Analysis

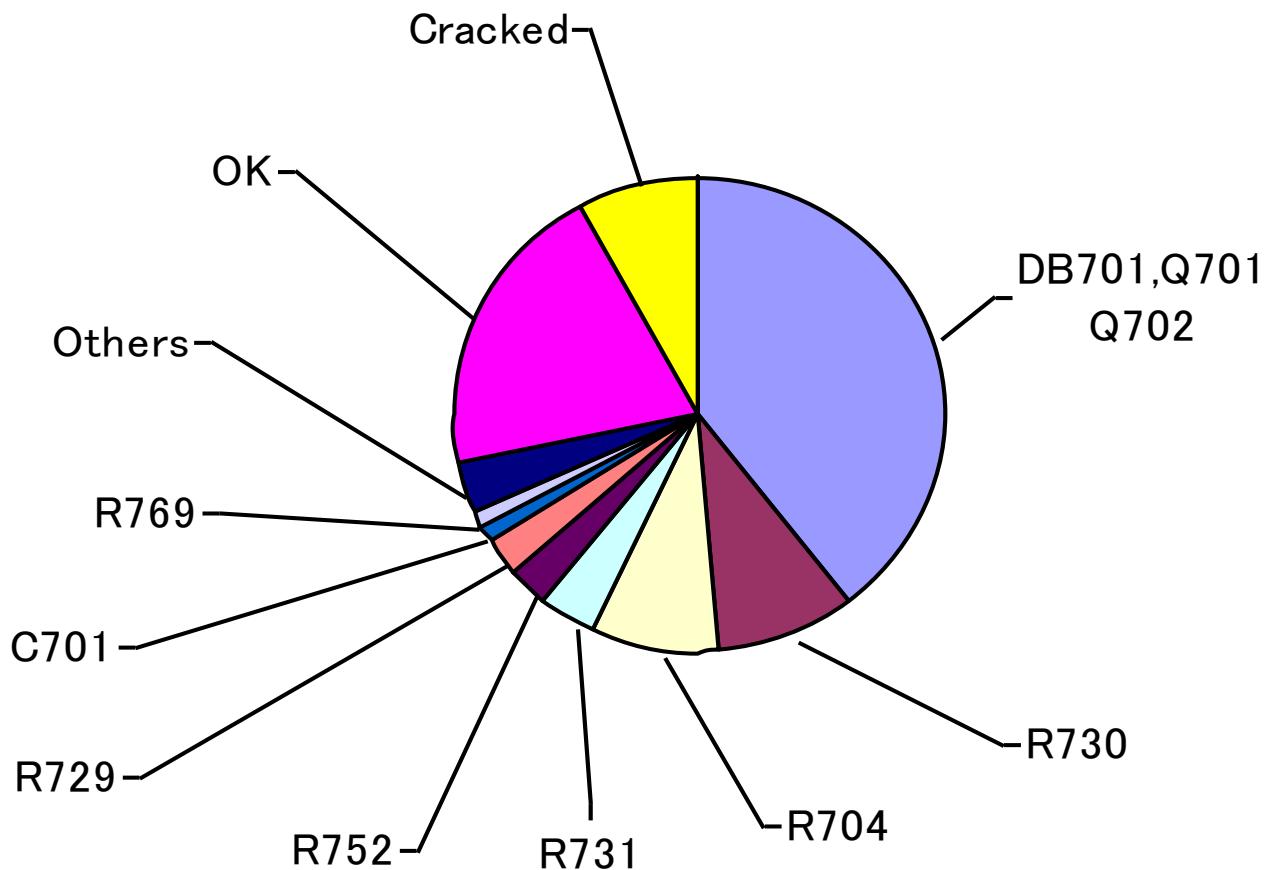

175 pieces repair data

S.H/CSD

Where Component Failed

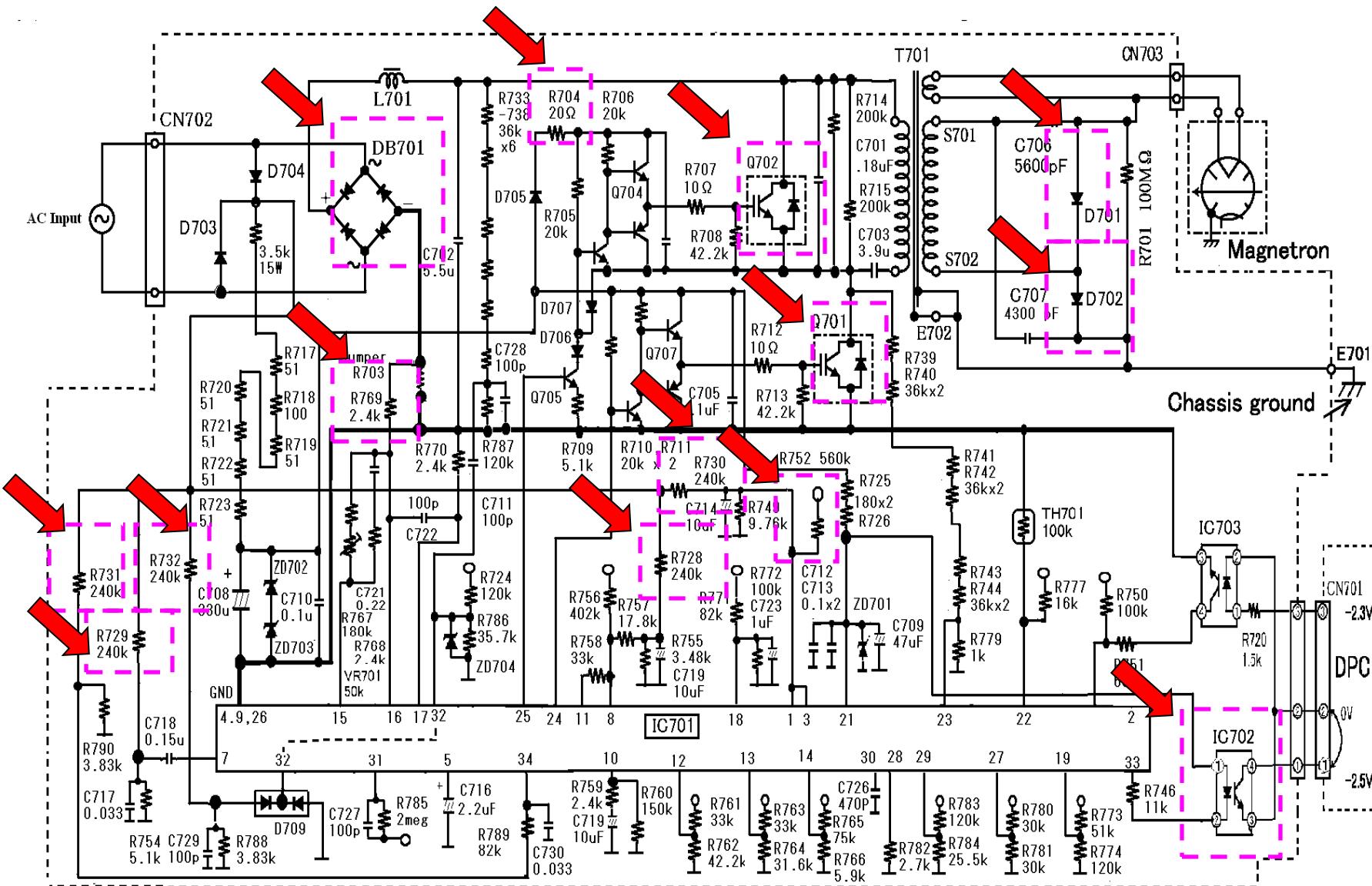


Up to this stage,

**you can fix over 95%
of faulty Inverter PCB**


but if not.....

More area to be checked is;


1. Cracking PCB

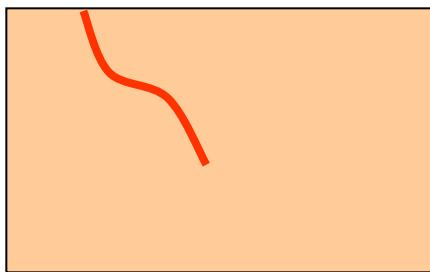


3. Cold solder joint

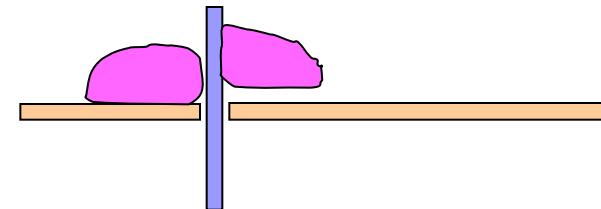

2. Cockroaches

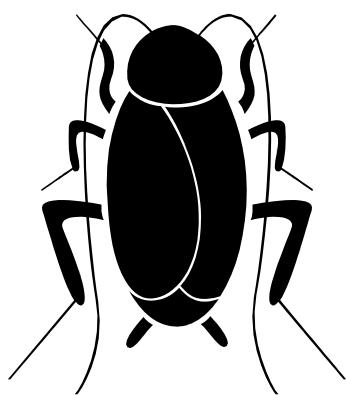

4. Broken/Missing component

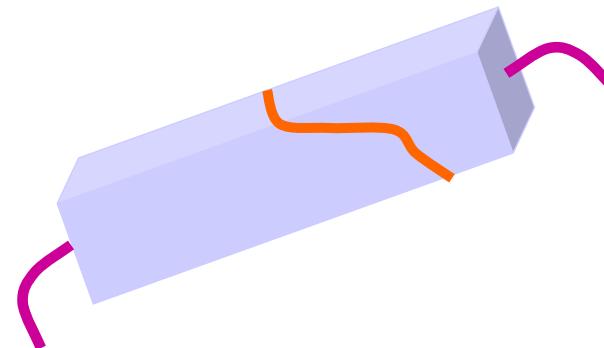

Before test Inverter

Make sure ;

1. Install it in its original place

DO NOT use extension cable

2. Install AIR GUIDE

If not, overheat and damage again

3. Secure grounding

4. Wiring Properly

5. Place water load and clear Inverter area

Input Amps Check



Thank You !!